
 


Programmierbare Logikbausteine

 

Übersicht über
verschiedene
PLD - Architekturen,
Systematisierung

Einführung




$$V_{O,max} = 40\%V_{DD} \text{ und } V_{I,max} = 60\%V_{DD}$$



NMOS

MOSFET (Metal-Oxide-Semiconductor-Field-Effect-Transistor)

x = "low" Pegel

 

x = "high" Pegel

 
 


PMOS


x = "high" Pegel



x = "low" Pegel

  


 CMOS Technologie (Complementary-Metal-Oxide-Semiconductor)



NOT Schaltung


Schaltbild

 

Wahrheitstabelle

x	T_1 T_2	f
0	on off	1
1	off on	0

NAND Schaltung

 

$$f = (x_1 \cdot x_2)' = \overline{x_1 \cdot x_2}$$

x_1	x_2	T_1	T_2	T_3	T_4	f
0	0	on	on	off	off	1
0	1	on	off	off	on	1
1	0	off	on	on	off	1
1	1	off	off	on	on	0

De Morgan's Law

$$\left[f(x_1, x_2, \dots, x_n, 0, 1, +, *) \right]' = f(x_1', x_2', \dots, x_n', 1, 0, *, +)$$

PUN $f = \overline{x_1 \cdot x_2} = (x_1 \cdot x_2)' = x_1' + x_2' = \overline{x_1} + \overline{x_2}$


PDN $\overline{f} = \overline{\overline{x_1 \cdot x_2}} = x_1 \cdot x_2$

NOR (NOT OR) Schaltung ???

PUN $f = \overline{x_1 \cdot x_2} = (x_1 + x_2)' =$

PDN $\overline{f} = \overline{(x_1 + x_2)'} =$

NOR (NOT OR) Schaltung

 

Minterms and sum of products

m	A	B	C	F ₀	F ₁	F ₂	F ₃
0	0	0	0	1	0	1	0
1	0	0	1	1	0	1	0
2	0	1	0	0	1	1	1
3	0	1	1	0	1	0	1
4	1	0	0	1	1	0	0
5	1	0	1	0	0	0	1
6	1	1	0	1	1	1	1
7	1	1	1	0	1	0	1


$$\begin{aligned}F_0 &= \sum m(0,1,4,6) = \\&= A'B'C' + A'B'C + AB'C' + ABC' = \\&= A'B'(C' + C) + AC'(B' + B) = \\&= A'B' + AC'\end{aligned}$$

$$F_1 = \sum m(2,3,4,6,7) = B + AC'$$


$$F_2 = \sum m(0,1,2,6) = A'B' + BC'$$

$$F_3 = \sum m(2,3,5,6,7) = AC + B$$

74XX Series

 


DIP (Dual-In-line-Package)

 

7404


74LS00 - Transistor-Transistor-Logic, TTL;
74HC00 - CMOS

74XX Series

 

$$f = x_1 \cdot x_2 + \overline{x_2} \cdot x_3$$

 
Dreieck beim Entwurf integrierter Digitalschaltungen




Verlustleistung

$$P_{\text{Verlustleistungsaufnahme}} = \sum \left[\begin{array}{c} \text{Anzahl der} \\ \text{Register} \end{array} \right] + [\text{Taktfrequenz}] + \left[\begin{array}{c} \text{Prozentsatz} \\ \text{an logischen} \\ \text{Gattern} \end{array} \right]$$

Computing in Space vs. Computing in Time

 

 

Computing in Space vs. Computing in Time

Räumliche Sequentialisierung


- Datenflussorientierung
- Parallelisierung
(Addition und
Subtraktion)
- Pipelining (Add/Sub
und Mul)

Zeitliche Sequentialisierung


- Kontrollflussorientierung
- Pipelining bei modernen
Mikroprozessoren (DSP)
auch möglich

Vergleich PLD mit anderen Entwurfsmethoden


ASIC – Kundenspezifische Schaltkreise

 

Systematisierung der Semi-Custom IC

 

Basic ROM Structure

 

- Conceptually ROM consists of a decoder and memory array;
- $2^n \times m$ ROM $\rightarrow m$ functions of n input variables (can store truth table with 2^n rows and m columns) – implementing combinatorial logic



Type of ROMs

There are 4 different ways of programming:


- **Mask programming:** done by the semiconductor company during the last fabrication process. Economical if large quantity is made;
- **PROM (Programmable ROMs):** PROM unit contains all the fuses intact giving all 1's in the bits of stored words. The fuses are blown by application of high-voltage pulse to the device through a special pin. A blown fuse defines a binary 0 state. This is an irreversible process. PROM programmers are available for this purpose.



Type of ROMs

- **Erasable PROM** – same as PROM but can be restructured to the initial state even though it has been programmed previously. When EPROM is placed under special ultra-violet light for a given period of time, the short wave radiation discharges internal floating gates that serve as the programmed connections (initialization);
- **Electrically-erasable PROM (E²PROM)**: same as EPROM except that erasing can be done with an electrical signal instead of ultra-violet light. The advantage is that the device can be erased without removing it from its socket.


Programmable Logic Array Structure

 

- m functions of n input variables;
- decoder $\rightarrow$ AND array;
- OR array $\rightarrow$ OR together product term needed to form output function

nMOS NOR Gate

 Logical gates are formed in array by connecting nMOS switching transistors between the column lines and the row lines.




X_1	X_2	nMOS	Z
0	0	off, off	1
0	1	off, on	0
1	0	on, off	0
1	1	on, on	0


$$Z = X_1' X_2' = (X_1 + X_2)' = \text{NOT-OR (NOR) Gate}$$

NOR-NOR Logic


$$F_0 = \sum m(0,1,4,6) = A'B' + AC'$$

 


nMOS PLA

 


AND-OR PLA

 


Programmable Logic Array - PLA

 


Programmable Array Logic - PAL

 

Programmable Array Logic - PAL

 

Unprogrammed PAL segment

 

Programmed PAL segment

Sequential Programmable Devices


- Digital systems are designed using flip-flops and gates. Since the combinatorial PLD consists of only gates, it is necessary to include external flip-flops when they are used in design;
- Sequential programmable devices include both gates and flip flops;
- In this way, the device can be programmed to perform a variety of sequential circuit functions;
- The major types are:
 - Sequential programmable logic devices (**SPLD**)
 - Complex Programmable Logic Device (**CPLD**)
 - Field Programmable Gate Array (**FPGA**)



Sequential Programmable Devices

- Sequential PLD is sometimes referred to as a simple PLD to differentiate it from the complex PLD.
- SPLD includes flip-flops within the integrated circuit chip in addition to the AND-OR array.
- A PAL or PLA is modified by including a number of flip-flops connected to form a register.
- The circuit output can be taken from the OR (combinational output) gates or from the outputs of flip-flops (registered output).
- Additional programmable connections are available to include the flip-flops (D or JK type) outputs in the product terms formed with the AND array.

Sequential Programmable Devices

 

Realization of the next-state equation:

$$Q^+ = D = A'BQ' + AB'Q$$




SPLD

- The configuration mostly used for SPLD is the combinatorial PAL together with D flip-flops;
- A PAL that includes flip-flops is referred to as a registered PAL;
- **Macrocell** - circuit that contains a sum-of-products combinational logic function and an optional flip-flop;
- A typical SPLD has from 8 to 10 macrocells within one ICE package.

Complex Programmable Logic Devices - CPLD

- The design of a digital system using PLD often requires the connection of several devices to produce the complete specification;
- For these type of applications, Complex Programmable Logic Devices (CPLD) are more suitable;
- A CPLD is a collection of individual PLDs on a single integrated circuit;
- A programmable interconnection structure allows the PLDs to be connected to each other in the same way that can be done with the individual PLD's.

 Complex Programmable Logic Devices - CPLD




General CPLD configuration

I/O Blocks provide the connection to IC pins.


Complex Programmable Logic Devices - CPLD

- The switch matrix receives inputs from the I/O block and directs it to the individual macrocells;
- Similarly, selected outputs from macrocells are sent to the outputs as needed;
- Each PLD typically contains from 8 to 16 macrocells;
- The macrocells within each PLD are usually fully connected. If a macrocell has unused product terms they can be used by other nearby macrocells;
- Different manufacturers use different approaches to make individual PLDs (sometime called *function blocks - FB*), the type of macrocell, I/O blocks and the programmable interconnection structure.


XILINX CPLD XC9500 Architecture

 


Function Block - FB

 




Macrocell of XC9500 CPLD

 

 


**Macrocell
Clock and
Set/Reset
Capability**


Product Term Allocator

   


FastCONNECT II Switch Matrix

 

I/O Block - IOB

 

ISP

 


Field Programmable Gate Arrays - FPGA

- The basic component used in **VLSI** design is the **gate array**. A gate array consists of pattern of gates fabricated in an area of silicon that is repeated thousands of times until the entire chip is covered with the gates;
- A typical programmable gate array (PGA) is an IC that contains an array of identical logic cells with programmable interconnections. The user can program the functions realized by each logic cell and the connections between cells. Such PGAs are often called FPGAs since they are field-programmable.
- A typical FPGA consists of an array of hundreds or thousands of logic blocks, surrounded by programmable input and output blocks and connected together via programmable interconnections.


XILINX XC3020

Logic Cell Array (LCA)

 


The interconnections between these blocks can be programmed by storing data in internal configuration memory cells.

Configuration Memory Cell

 

The configuration memory cells are programmed after power has been applied and logic function and interconnections are retained until the power exists. During configuration, when a WRITE signal is applied to the pass transistor, DATA is stored in the cell. Each connection point in the LCA has an associated memory cell, and the data stored in that cell determines whether the connection is made or not.

FPGA Application Trends

 

Top-level Architecture of Present Generation Xilinx FPGA

Delay Locked Loop (DLL)

Clock management
Multiply clock
Divide clock
De-skew clock

Configurable Logic Block (CLB)

Logic and
Distributed RAM

SelectI/O™ Technology

Chip to Backplane
PCI 33MHz 3.3V
PCI 33MHz 5.0V
PCI 66MHz 3.3V
GTL, GTL+, AGP


Chip to Memory
HSTL-I, HSTL-III
HSTL-IV
SSTL3-I, SSTL3-II
SSTL2-I, SSTL2-II
CTT

Chip to Chip
LVTT, LVCMOS

Block Memory

True Dual-Port™
4K bit RAM


4Kx1
2Kx2
1Kx4
512x8
256x16

 

Top-level Architecture of Present Generation Xilinx FPGA

- Configurable logic blocks (CLBs)
 - Implement logic and memory here!
 - I/O blocks
 - Communicate with other chips
 - Choose from 16 signal standards
 - Block RAM
 - On-chip memory for higher performance
- Clocks and delay locked loops (DLLs)
 - Synchronize to clock on and off chip
 - Rich interconnect resources
 - Three-state internal buses

Configurable Logic Blocks - CLB

 


- Combinational logic generated in a lookup table (LUT)
 - Any function of available inputs
- Generates any function of its inputs
 - Typically 4 inputs
- Logically equivalent to a 16x1 ROM

Inputs

0000
0001
0010
0011


Output

0
1
1
0

 


$$Y = X_0 \text{ xor } X_1$$

CLB – Slice (2 LC)

 


Block RAM

 


Width	Depth	ADDR Bus	Data Bus
1	4096	ADDR<11:0>	DATA<0>
2	2048	ADDR<10:0>	DATA<1:0>
4	1024	ADDR<9:0>	DATA<3:0>
8	512	ADDR<8:0>	DATA<7:0>
16	256	ADDR<7:0>	DATA<15:0>

I/O Block - IOB

 


Programmable Routing Matrix

General-purpose Interconnects

 


 Direct Interconnects Between Adjacent CLBs



Programmable Routing Matrix

Vertical and Horizontal Long Lines

 

Hersteller von PLD

Hersteller	PLD	CPLD	FPGA
Actel (incl. Gatefield)			SX/SX-A-Familie MX-Familie ProASIC-Familie eX-Familie
Altera		MAX7000-Familie MAX9000-Familie FLEX6000-Familie FLEX10K-Familie APEXII-Familie APEX20K-Familie	
Atmel	PAL-kompatible SPLD	ATF-Familie	AT40K-Familie AT94K-Familie
Cypress	PALCE	Delta39K Ultra37K Flash370i	
Lattice (Vantis von AMD)	ispGAL GAL SPLD	5000-Familie ispMACH4A 2000-Familie 8000-Familie	
Lucent			ORCA-Familie
Quicklogic			pASIC-Familie Eclipse-Familie
Xilinx		XC9500 CoolRunner	VIRTEX-Familie Spartan-Familie XC5000-Familie XC3000-Familie XC5200-Familie